

Name: Binod Pathak

Group: L4CG5


Email Address: np03cs4a220028@heraldcollege.edu.np

1. Draw the logic diagram of the following gates using logsim and complete the Truth tables.

a) AND

Answer:

A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

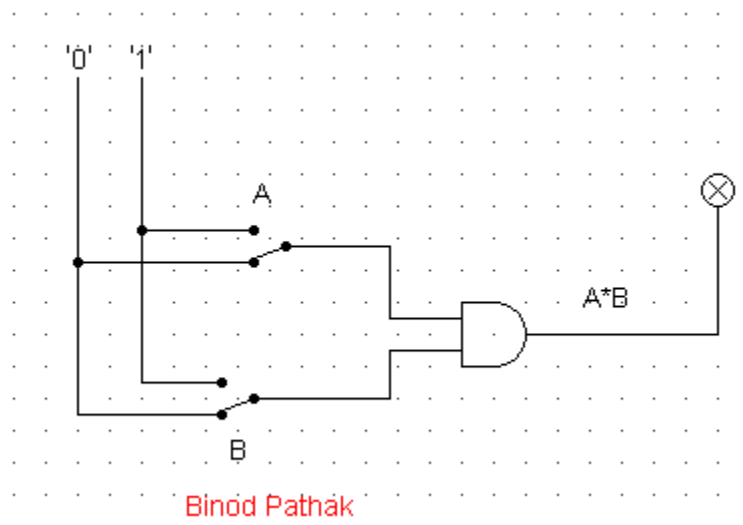

b) NOR

Answer:


A	B	A.B
0	0	1

Name: Binod Pathak

Group: L4CG5

Email Address: np03cs4a220028@heraldcollege.edu.np

0	1	0
1	0	0
1	1	0

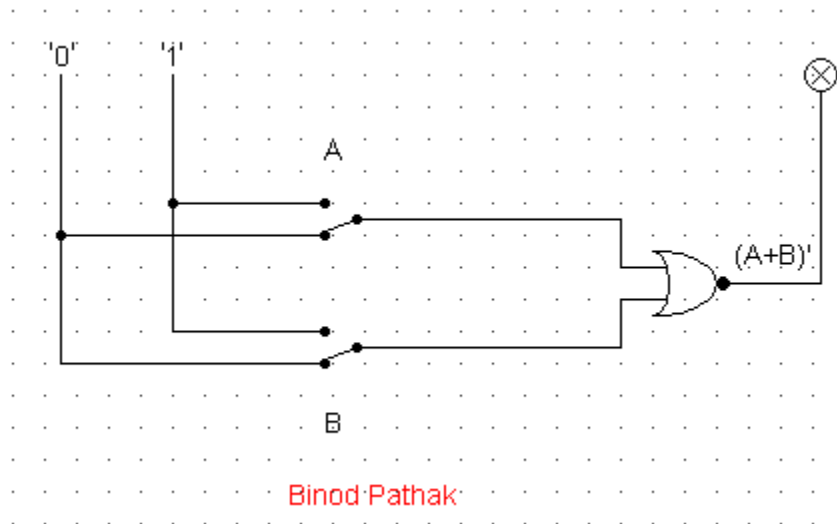


c) OR
Answer:

A	B	A.B
0	0	0
0	1	1
1	0	1
1	1	1

Name: Binod Pathak

Group: L4CG5

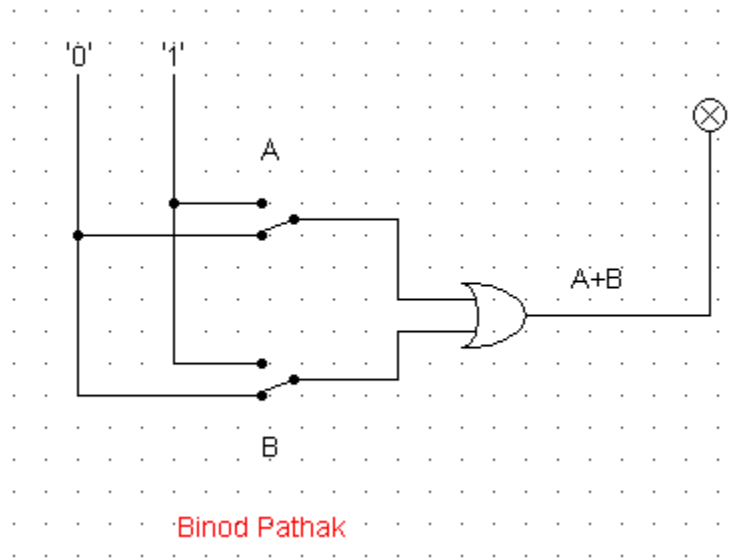Email Address: np03cs4a220028@heraldcollege.edu.np



d) NAND (using NOT and AND)


Answer:

A	B	A.B
0	0	0
0	1	1
1	0	1
1	1	1

Name: Binod Pathak

Group: L4CG5

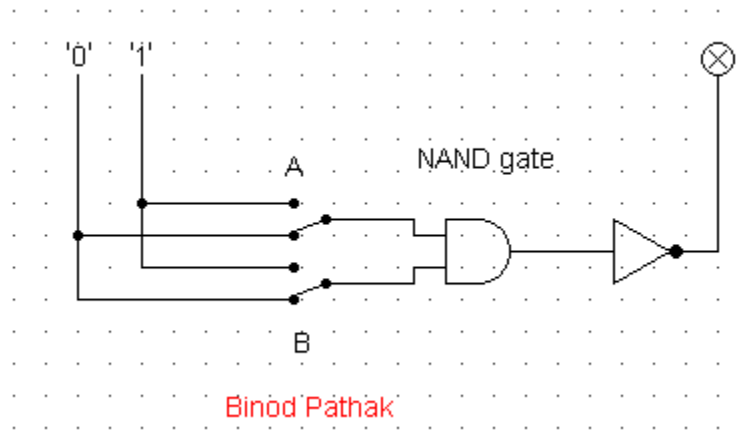Email Address: np03cs4a220028@heraldcollege.edu.np



e) XOR using AOI

Answer:


A	B	$(AB' + A'B)$
0	0	0
0	1	1
1	0	1
1	1	0

Name: Binod Pathak

Group: L4CG5

Email Address: np03cs4a220028@heraldcollege.edu.np

A	B	$!(A+B)$	$!A \cdot !B$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

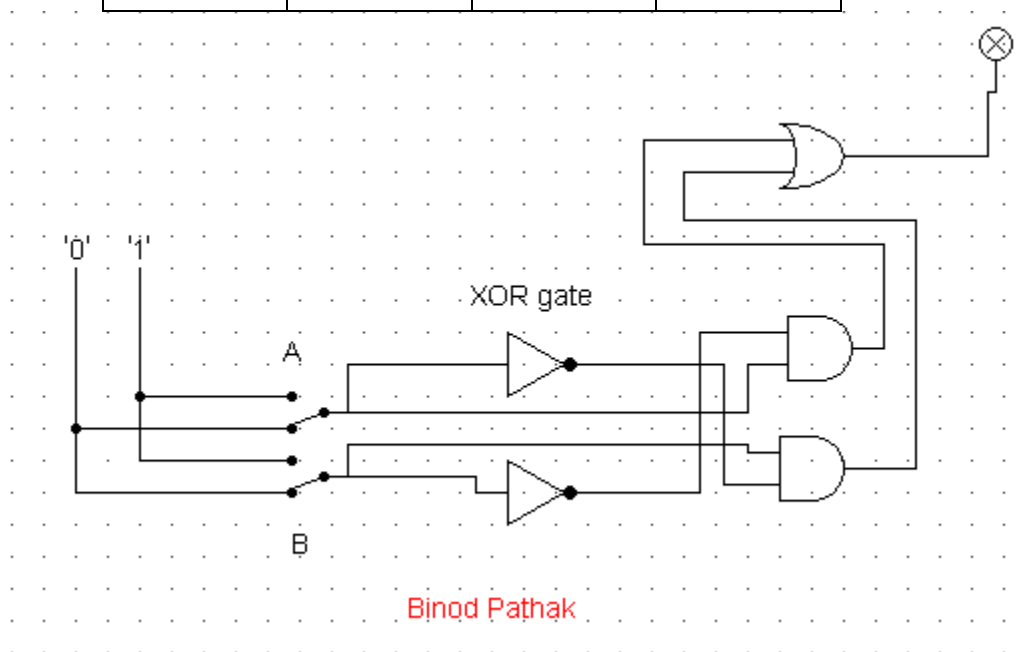

2. Use LogSim to build the equivalent circuit for the following Boolean equations.
Prove that the expressions are equivalent by computing truth table.


$$!(A + B) = !A \cdot !B$$

Answer:

Name: Binod Pathak

Group: L4CG5

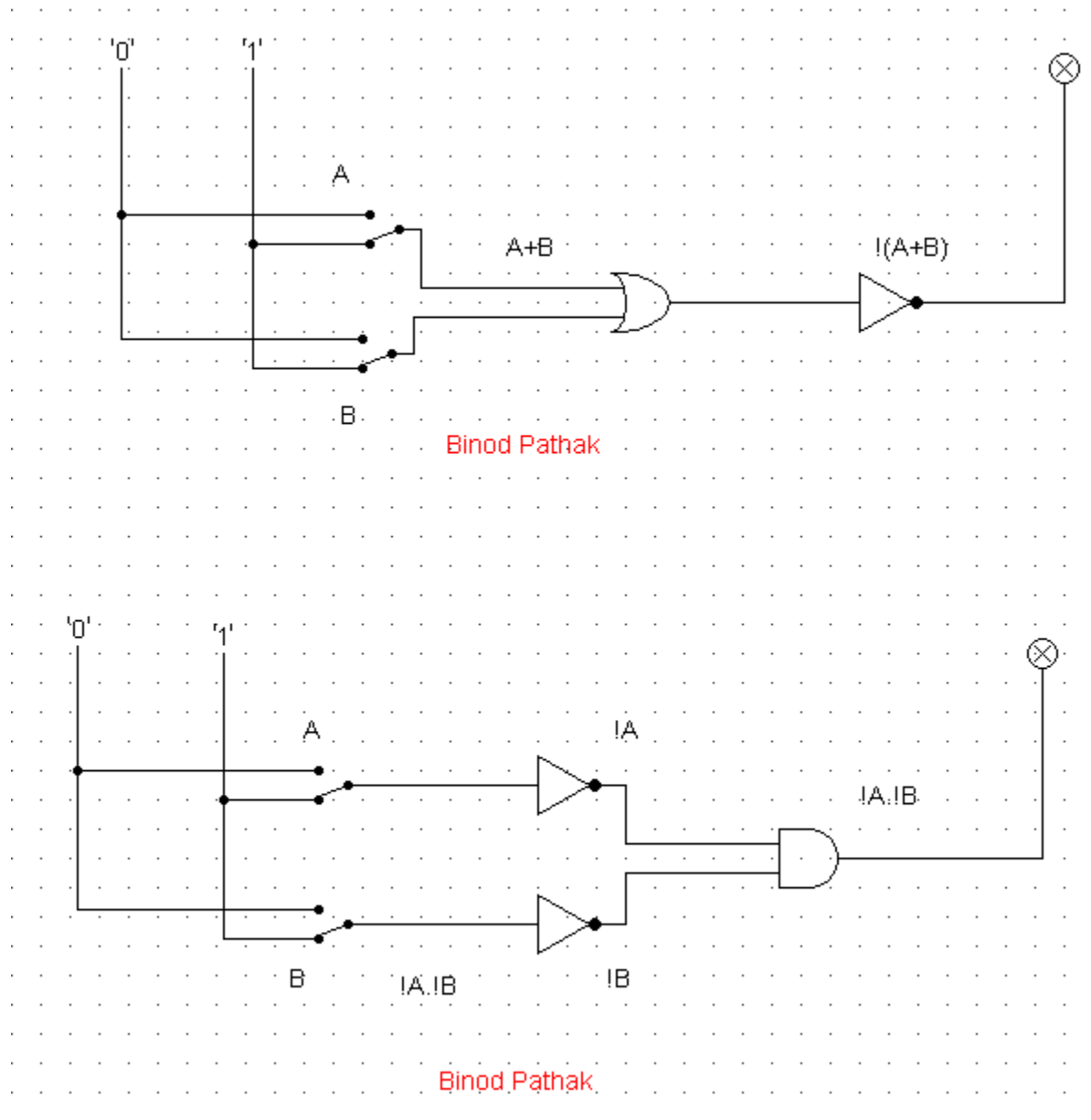Email Address: np03cs4a220028@heraldcollege.edu.np




3. Draw the following circuit of half adder using LogSim.


Name: Binod Pathak

Group: L4CG5

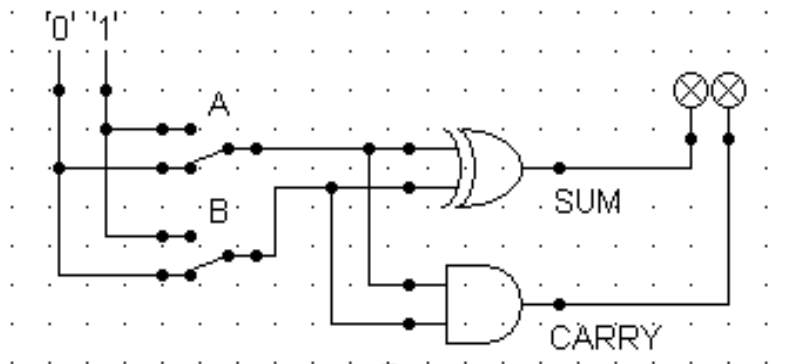Email Address: np03cs4a220028@heraldcollege.edu.np



Answer:

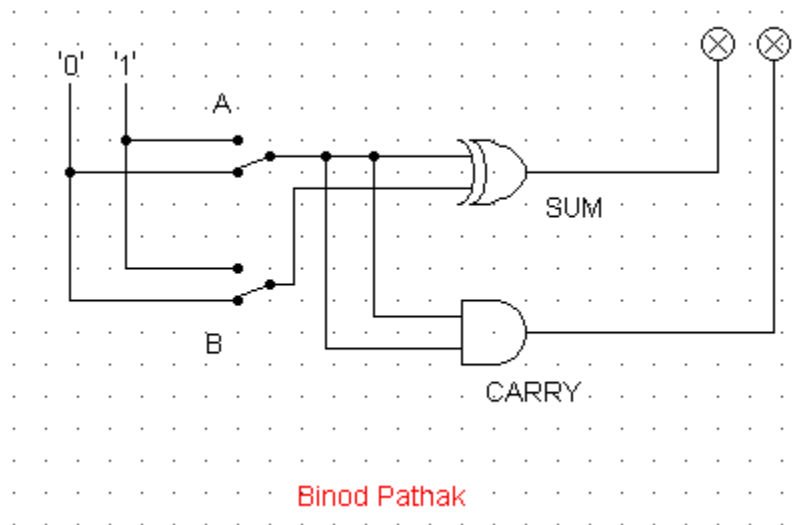

4. Draw full adder using Logsim and construct truth table.

Answer:

Group: L4CG5


a. $AB+C$

Answer:

Name: Binod Pathak

Group: L4CG5

Email Address: np03cs4a220028@heraldcollege.edu.np

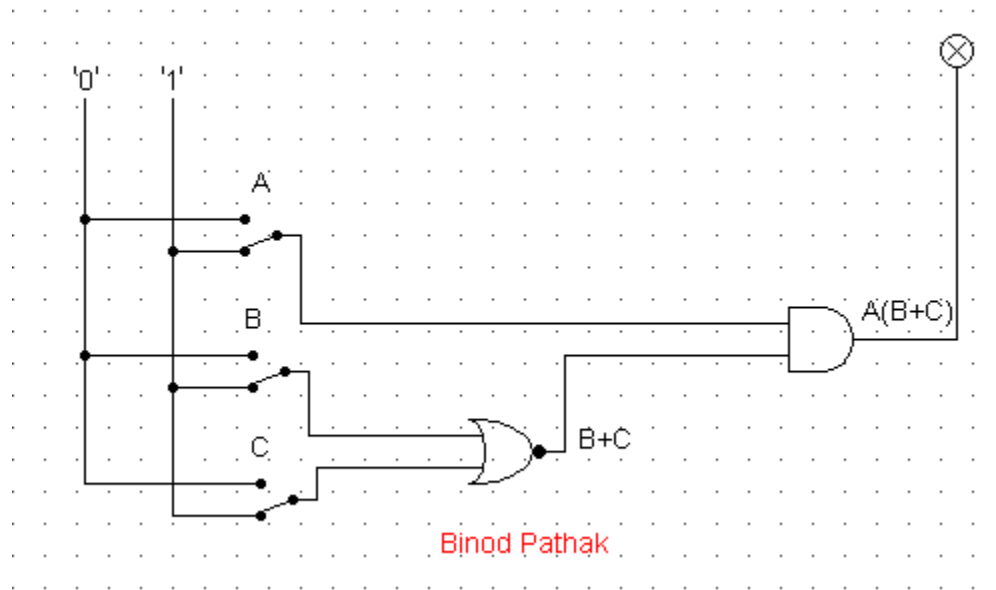c. $X'Y'Z'$

Answer:

