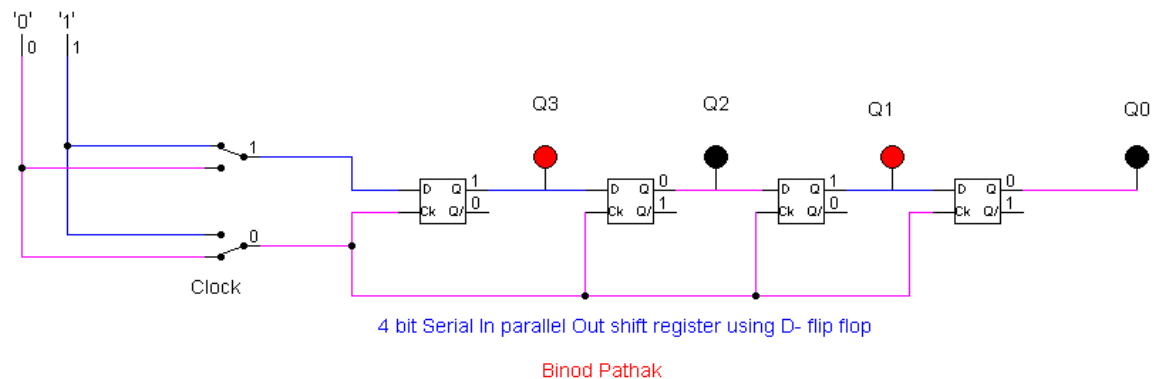


1. Construct 4 bit Serial In parallel Out shift register using D- flip flop. Explain the Working mechanism of the circuit taking Serial input 1010. Also draw the timing diagram according to the given input.

**Answer:**



**Answer:**

Clock	Input	Q3	Q2	Q1	Q0
	Initial	0	0	0	0
↑	0	0	0	0	0
↑	1	1	0	0	0
↑	0	0	1	0	0
↑	1	1	0	1	0


**Describe:** The circuit shown in the following diagram outputs parallel data while accepting serial input. The clock values change to 1 and the value is delivered to Q3 when the value 0 is used as input. The clock values then change from 1 to 0 and back to 1 as input 1 is used. Q3's value is then transferred to Q2 and Q3 is then set to 1. After that, input 0 is used, the clock values switch from 1 to 0 to 1 again, Q2's value is transferred to Q1, and Q3's value is determined by input 1's value. The clock values are then altered to 0 and 1, Q2 becomes Q1, Q1 becomes Q0, and Q3 is given the value 1.

**Timing Diagram:**

## Workshop - 5

### Question :- 1


### Timing Diagram :-

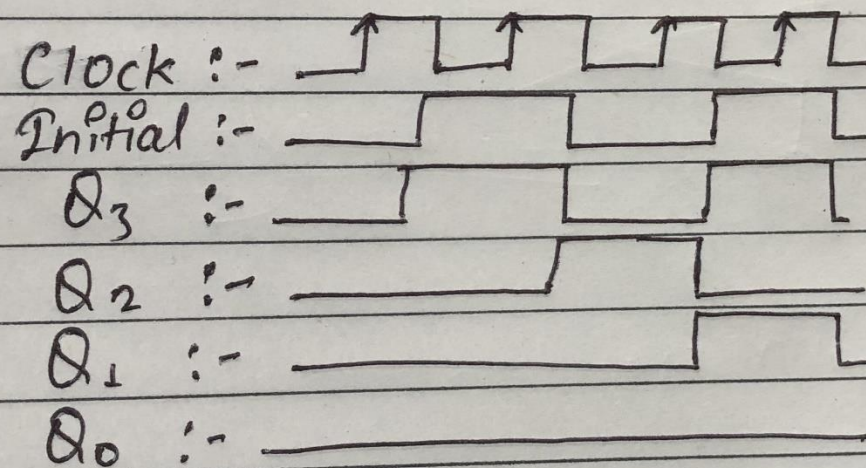

Binod Pathak

2. Design a 3 bit counter using Toggle D-flip flop and draw the timing diagram.

**Answer:**

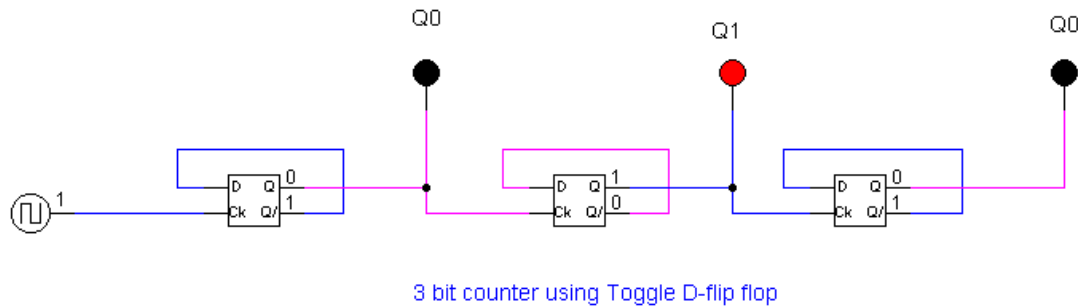


Binod Pathak


**Table:**

Clock Transition	Q2	Q1	Q0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

**Timing Diagram:**

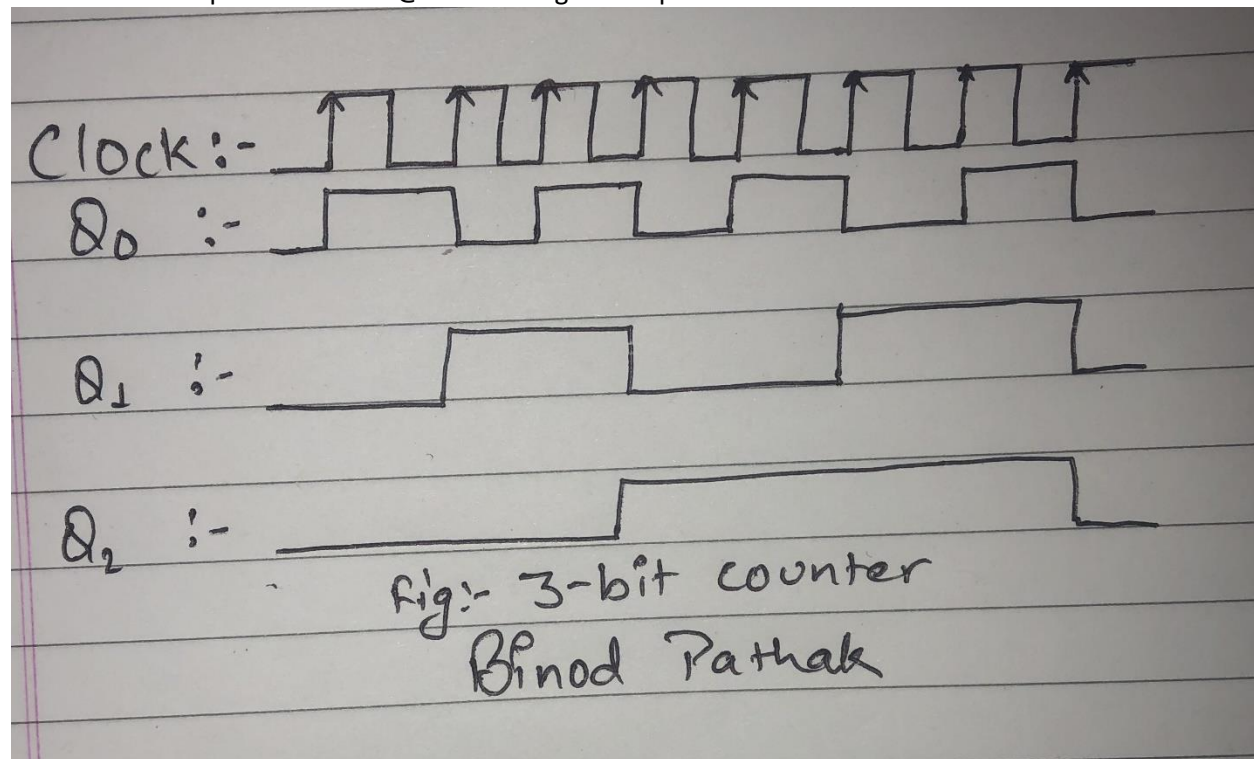

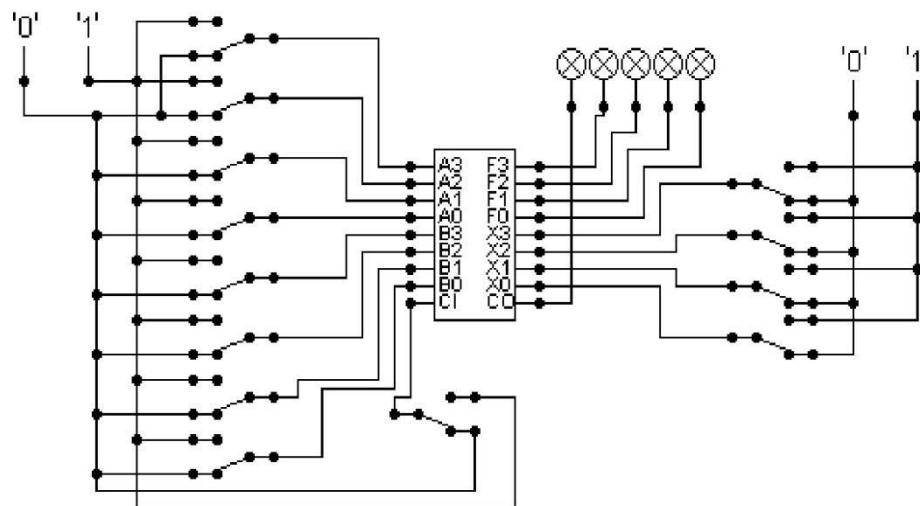3. Load alu.cct file from the logsim folder. The circuit should look like this



The circuit behaves like a simple arithmetic logic unit. The inputs A0-A3 represent a 4 bit binary number. Inputs B0-B3 represent another binary number. A0 and B0 are the least significant bits respectively. The following table details the functions supported by the chip. All other control lines = 0.

Function	Add	Subtract
X3-X0	1010	1011

Binod Pathak

Group: L4CG5

Email Address: np03cs4a220028@heraldcollege.edu.np


i) Use A = 15 and B = 7

ii) Use A = 13 and B = 9

Write the corresponding result of the operations. Manually provide each operation has provided the correct result.

**Answer:**


i) Use A = 15 and B = 7

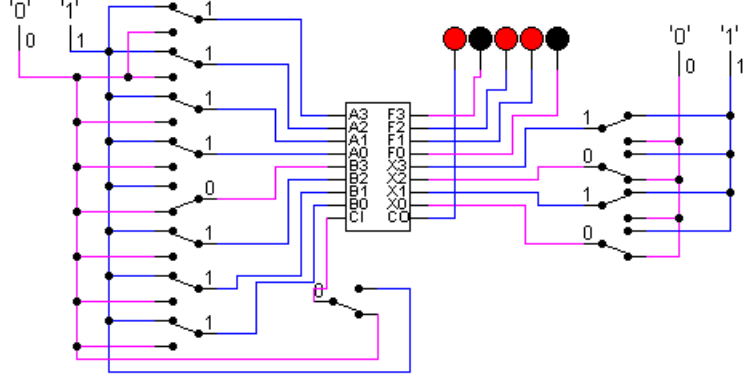Inputs	Function	Result
A = 15 = 11 1 1 B = 7 = 011 1	Add - 1010	Result = 1011  <p>Binod Pathak</p>

Binod Pathak

Group: L4CG5

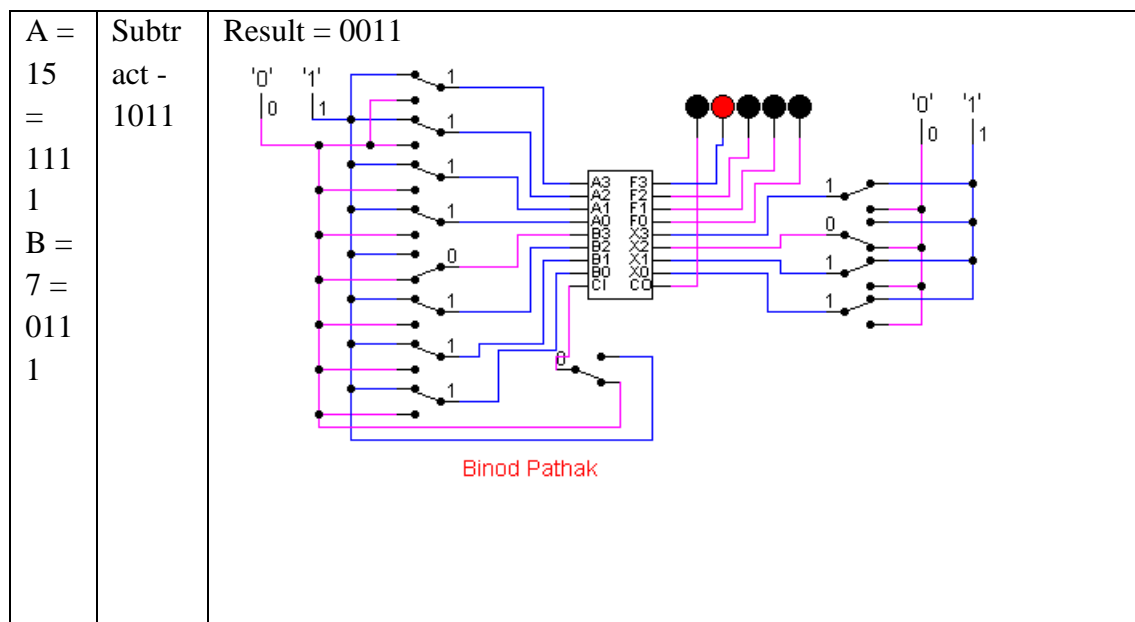Email Address: np03cs4a220028@heraldcollege.edu.np





Binod Pathak

Group: L4CG5

Email Address: np03cs4a220028@heraldcollege.edu.np

ii) Use A = 13 and B = 9

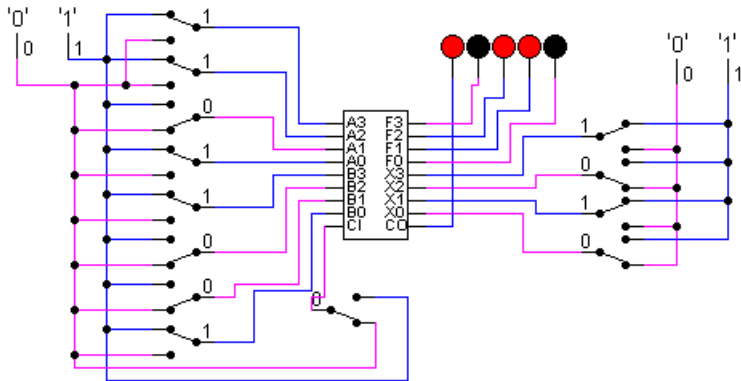Use A = 13 and B = 9 Inputs	Function	Result
A = 13 = 1101 B = 9 = 1001	Add - 1010	Sum = 1011 Carry = 1 
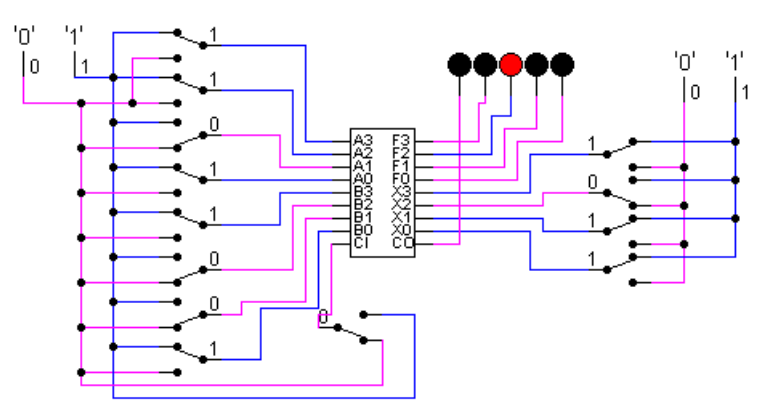
<p>A = 15 = 1111 B = 7 = 0111</p>	<p>Subtra ct - 1011</p>	<p>Difference = 0001 Borrow = 1</p>  <p>Binod Pathak</p>
---	---------------------------------	--